

"This is the differential equation describing the current:"

$$\text{"emf} + iR + L(di/dt) = 0"$$

"separate the variables:"

$$\text{"di}/(i + \text{emf}/R) = -(R/L) dt"$$

"integrate:"

$$\int_{i_0}^i \frac{1}{i + \frac{\text{emf}}{R}} di = \int_0^t -\frac{R}{L} dt$$

"solve:"

$$\text{LN}(R \cdot i + \text{emf}) - \text{LN}(R \cdot i_0 + \text{emf}) = -\frac{R \cdot t}{L}$$

"solve for i as a function of t:"

$$\left[i = \frac{\hat{e}^{-R \cdot t/L} \cdot (R \cdot i_0 + \text{emf})}{R} - \frac{\text{emf}}{R} \right]$$

"plug in some numbers:"

$$\text{"R=0.09 L=0.0002 i0=2.7 emf=12"}$$

$$\left[i = \frac{4081 \cdot \hat{e}^{-450 \cdot t}}{30} - \frac{400}{3} \right]$$

"use the above to plot a graph of i vs t"

"find the value of t for which i=0:"

$$\left[t = \frac{\text{LN}\left(\frac{4081}{4000}\right)}{450} \right]$$

$$\left[t = 4.45504340083 \cdot 10^{-5} \right]$$